

# Summative Assessment for Electrical Circuit Lesson:

Describe the purpose of each item:

Battery:

Light Bulb:

Copper Wire:

What does the word circuit mean to you? (why?)

What is the difference between an open and a closed circuit?

What can be used as evidence to show when a circuit is closed or open?