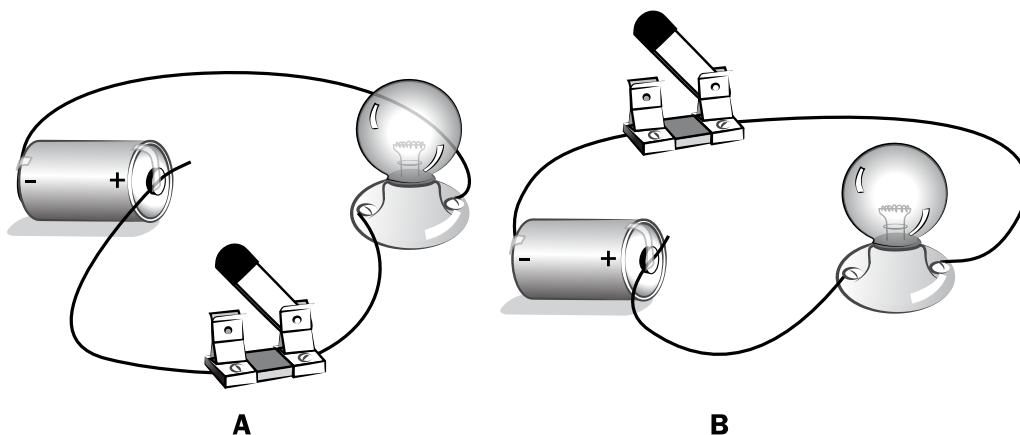


Where Do I Put the Switch?



Three students are building a complete circuit in their science class. They want to turn the lightbulb on and off with a switch. They disagreed about where the switch should go. This is what they said:

Keenan: I think the switch needs to be between the + end of the battery and the bulb, like Circuit A.

Felicia: I think the switch needs to be between the – end of the battery and the bulb, like Circuit B.

Bruno: I think it doesn't matter which side of the battery the switch is on.

With which student do you agree the most? _____ Explain why you agree.
